	С, мкФ				Изм	лери	ТЬ		Рассчитать									
Nº			Р, Вт	·	U, B	U _R ,	B U _L , B	U _C , B	R, Ом	X _C , Ом	φ,	, °	Z, Ом	X _L , Ом	Х, Ом	S, B*	А <mark>О, вар</mark>	cosφ
1.	2. C _p -30 140 2 3. C _p -20 150 2 4. C _p -10 160 2		2442	11.65	220	209	.6 215.1	281.6	17.991	18.464	0.3	307	18.884	24.172	5.708	2563	.0 19.48	0.953
-						214	.7 220.3	253.6	17.993 1 18.007 1	18.466	0.2	218	18.441	22.448 20.941	2.486 2 1.181 2 0.025 2	2664.2 2681.8 2684.0	.6 13.75	0.976
						217	.9 223.5			18.456	0.1	.37	18.167				.2 8.65	0.990
4.			2677	12.19		219	.5 225.1			18.466	0.0)66	18.048 19 18.033 18	19.647			.8 4.12	0.998 1.001
5.	P											-						
_	$C_p + 10 180$ $C_p + 20 190$						_		18.000 1									
-								+ +				_		3.107 16.543				
	C _p +30				ļ			_									.6 -9.55	
9.	C _p +40	210	2591	12.00		215	.9 221.5	179.5	17.992	18.458	-0.1	192	18.333	14.958	4.958 -3.500		.0 -12.12	0.981
	№ С, ми						Изм	ерит	ь			Рассчитать				ГЬ		
Nº			ζФ	P, B	r T	Ј, В	I, A	I _{R'} B	I _L , B	$I_{C'}$	В	Y,	См	G, См	В,	Ом	cosφ	
1.	C _p -	40	130	2771	_		12.91	12.22	11.92	2 9.0	9	0.0)587	0.0555	0.0	129	0.976	
2.	C_{p}	C _p -30	140	2785			12.84	12.22	11.92	2 9.7	9	0.0	0584	0.0555	0.0	097	0.986	
3.	C_{p}	20	150	2805	5		12.80	12.22	11.92	2 10.4	9	0.0	0582	0.0555	0.0	065	0.996	
4.	C_{p}	10	160	2814	1		12.81	12.22	11.92	2 11.1	9	0.0	0582	0.0555	0.0	033	0.999	
5	. C	p	170	2833	3	20	12.86	12.22	11.9	2 11.8	88	0.0)585	0.055	0.0	002	1.001	
6.	C_{p}	-10	180	2846	5 4 4		12.96	12.22	11.92	2 12.5	8	0.0	0589	0.0555	6.0	030	0.998	
7.	C_{p}	-20	190	2865			13.09	12.22	11.92	2 13.2	8	0.0	0595	0.0555	5 -0.0	062	0.995	
8.	C_{p}	-30	200	2884			13.26	12.22	11.92	2 13.9	7	0.0	0603	0.0555	5 -0.0	093	0.989	
9.	C_{p}	-40	210	2904		[13.48	12.22	11.92	2 14.6	57	0.0	0613	0.0555	5 -0.0	125	0.979	
10	C_{p}	-50	220	2924			13.74	12.22	11.92	2 15.3	37	0.0	0624	0.0555	6-0.0	157	0.969	